

BT-104 – BASIC ELECTRICAL & ELECTRONICS ENGINEERING

UNIT-WISE 5 MOST IMPORTANT QUESTIONS

- Based on **PYQ repetition + syllabus weightage + exam probability**
- Strictly **5 units** (no extra / no mismatch)
- RGPV-oriented (numerical + theory mix)

PYQs analysed from: **May-2019, Nov-2019, Jun-2020, Dec-2023, Jun-2022, Nov-2022, Jun-2023, Dec-2024, Jun-2025**

UNIT-I: DC CIRCUITS

👉 **Most repeated unit (numericals every year)**

Top 5 Important Questions

1 State and explain Kirchhoff's Current Law (KCL) and Voltage Law (KVL). Solve a numerical.

Asked in: **2019, 2022, 2025**

2 Explain Superposition Theorem and solve a circuit using it.

Asked in: **2019, 2020, 2023, 2025** 🔥

3 Find current/voltage using Mesh or Nodal Analysis.

Asked in: **2020, 2023, 2024, 2025**

4 Explain and solve problems on Star-Delta / Delta-Star transformation.

Asked in: **2019, 2020, 2023, 2024**

5 Explain dependent and independent sources with neat sketches.

Asked in: **2023, 2024**

UNIT-II: AC CIRCUITS

👉 Guaranteed numerical + theory every year

Top 5 Important Questions

1 Define RMS value, average value, form factor and peak factor of AC quantity.

Asked in: 2020, 2022, 2023, 2024, 2025 🔥

2 Solve numericals on RLC series circuit (Impedance, current, power factor).

Asked in: 2022, 2023, 2024, 2025

3 Explain active, reactive and apparent power in AC circuits.

Asked in: 2019, 2020, 2022, 2023

4 Three-phase balanced star/delta system – line & phase values with phasor diagram.

Asked in: 2020, 2022, 2024 🔥

5 Explain resonance in RLC circuit (series/parallel).

Asked in: 2019, 2023

UNIT-III: MAGNETIC CIRCUITS & TRANSFORMER

👉 Transformer = fixed long question

Top 5 Important Questions

1 Explain construction, working principle and EMF equation of single-phase transformer.

Asked in: 2019, 2020, 2023, 2025 🔥

2 OC & SC test on transformer and determination of equivalent circuit parameters.

Asked in: 2020, 2023, 2024

3 Losses in transformer and efficiency calculation numericals.

Asked in: 2019, 2022, 2025

4 Explain magnetization characteristics of ferromagnetic materials (B-H curve).

Asked in: 2020, 2023, 2024

5 Define self-inductance & mutual inductance. Derive their relation.

Asked in: 2022, 2023

UNIT-IV: ELECTRICAL MACHINES

👉 Mostly theory + diagrams

Top 5 Important Questions

1 Explain construction and working principle of DC machine with diagram.

Asked in: 2019, 2024, 2025

2 Explain principle of operation of 3-phase induction motor.

Asked in: 2020, 2022, 2023, 2025 🔥

3 Explain torque-slip characteristics of induction motor.

Asked in: 2023, 2024

4 Explain losses occurring in electrical machines.

Asked in: 2019, 2023, 2024

5 Numericals on slip, synchronous speed, rotor speed.

Asked in: 2023, 2024

UNIT-V: BASIC ELECTRONICS

👉 Short notes + diagrams compulsory

Top 5 Important Questions

1 Draw and explain V-I characteristics of PN junction diode.

Asked in: 2020, 2023, 2025 🔥

2 Explain working of BJT and its configurations (CE/CB/CC).

Asked in: 2019, 2022, 2023, 2024

3 Explain Half adder and Full adder with truth table.

Asked in: 2020, 2022, 2024

4 Explain JK flip-flop / RS flip-flop with logic diagram.

Asked in: 2019, 2020, 2023, 2024

5 Explain De-Morgan's Theorem with example.

Asked in: 2019, 2020, 2022, 2024

EXAM STRATEGY (VERY IMPORTANT)

Unit	Importance
Unit I (DC Circuits)	★★★★★
Unit II (AC Circuits)	★★★★★
Unit III (Transformer)	★★★★★
Unit IV (Machines)	★★★
Unit V (Electronics)	★★★

👉 **Units I + II = 50% paper numericals**

👉 **Transformer + Electronics = easy theory marks**

FULL PREDICTED MODEL PAPER (2025)

Time: 3 Hours

Maximum Marks: 70

Instructions

1. Attempt **any FIVE** questions.
2. All questions carry **equal marks (14 marks each)**.
3. Draw neat diagrams wherever required.
4. Assume suitable data if required.

Q1. (UNIT–I: DC CIRCUITS)

a) State and explain Kirchhoff's Laws.

Apply KVL to find the current in a given DC circuit. (7)

b) Explain the Superposition Theorem.

Solve a simple circuit using superposition method. (7)

Q2. (UNIT–I: NETWORK THEOREMS)

a) Explain Thevenin's Theorem with necessary steps. (7)

b) Find the Thevenin equivalent circuit across given terminals and calculate load current. (7)

Q3. (UNIT–II: AC CIRCUITS)

a) Define RMS value, average value, form factor, and peak factor of AC quantity. (7)

b) An RLC series circuit is connected to AC supply.

Find impedance, current, power factor and power consumed. (7)

Q4. (UNIT–II: THREE-PHASE AC CIRCUITS)

a) Explain balanced three-phase system with neat phasor diagram. (7)

b) Derive the relation between line and phase quantities for

i) Star connection

ii) Delta connection (7)

Q5. (UNIT–III: TRANSFORMER)

- a) Explain construction and working principle of a single-phase transformer with diagram. (7)
- b) Derive the EMF equation of a transformer. (7)
-

Q6. (UNIT–III: TRANSFORMER PERFORMANCE)

- a) Explain losses in transformer and methods to improve efficiency. (7)
- b) A transformer has given losses.
Calculate **efficiency at full load**. (7)
-

Q7. (UNIT–IV: ELECTRICAL MACHINES)

- a) Explain construction and working principle of DC machine with diagram. (7)
- b) Explain working principle of three-phase induction motor.
Draw **torque–slip characteristics**. (7)
-

Q8. (UNIT–V: BASIC ELECTRONICS)

- a) Draw and explain V-I characteristics of PN junction diode. (7)
- b) Write short notes on any TWO: (7)
- BJT and its configurations (CE, CB, CC)
 - Half adder and Full adder
 - JK flip-flop
 - De-Morgan's Theorem

- Applications of induction motor
-